



$$I_1 - I_2 = I \tanh\left(\frac{1}{2} \frac{q_e}{kT} \frac{V_m}{T_m} t\right)$$

$$\approx I \sin\left(\frac{\pi}{2} \frac{t}{T_m}\right) \quad \text{for } -T_m \leq t \leq T_m$$

Similarly, again as an intuitive ‘fitting’, suppose we chose the peak value of the sinusoid and the value of the hyperbolic tangent to be the same at $t = T_m$ (note that $\tanh(\pi/2) = 0.92$). (This reduces the initial slope of the sinusoid about 5%, a sophistic adjustment ignored here.)

This assures the two functions have equal values at the origin and at their peak, and both start with very nearly the same slope; a sort of general continuity in nature suggests that the relationship between corresponding intermediate points is improved in consequence.

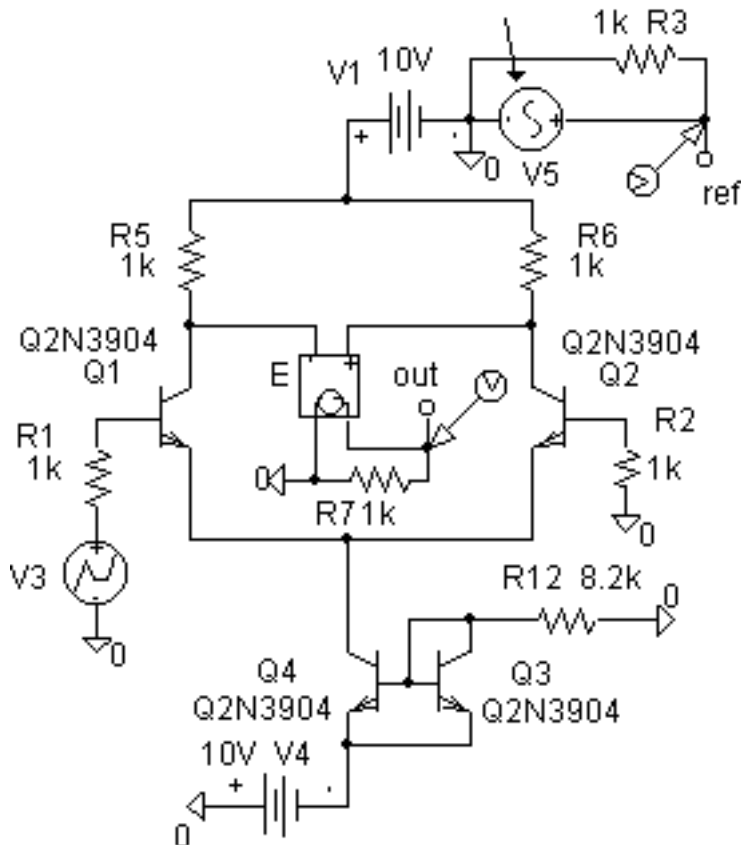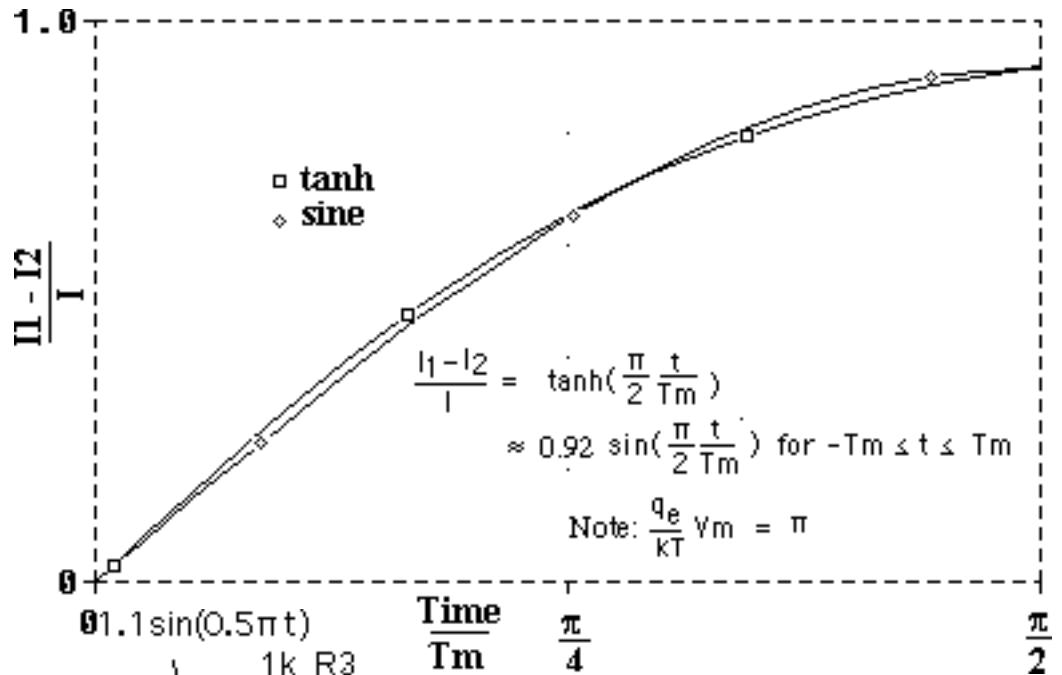
The two functions are compared in the figure to the left; even the unrefined approach taken is seen to yield a surprisingly good approximation. Note the ‘crossover’ of the two functions.



To test the fit in practice the differential amplifier test circuit drawn below was assembled. The base voltage is a triangular waveform with varying between ± 85 millivolts (corresponding to the approximate slope assumption described before), and with a (more or less arbitrarily chosen) normalized period of 4 seconds. Rather than monitoring the differential currents the differential collector voltage is used. The emitter bias current provided by Q4 is $(10 - 0.7)/8.2 = 1.13$ ma. For latter purposes of comparison a ‘reference’ sinusoidal voltage source with amplitude 1.1 ($1.1\text{ma} \cdot 1\text{k}$) is defined at the upper right of the circuit. As a simplification a voltage-controlled voltage source E is used to extract the differential collector voltage.

A PSpice computation of the differential output voltage is plotted below, and compared to the sinusoidal reference. Total harmonic distortion of the output waveform (10

harmonics) is computed to be 1.2%.

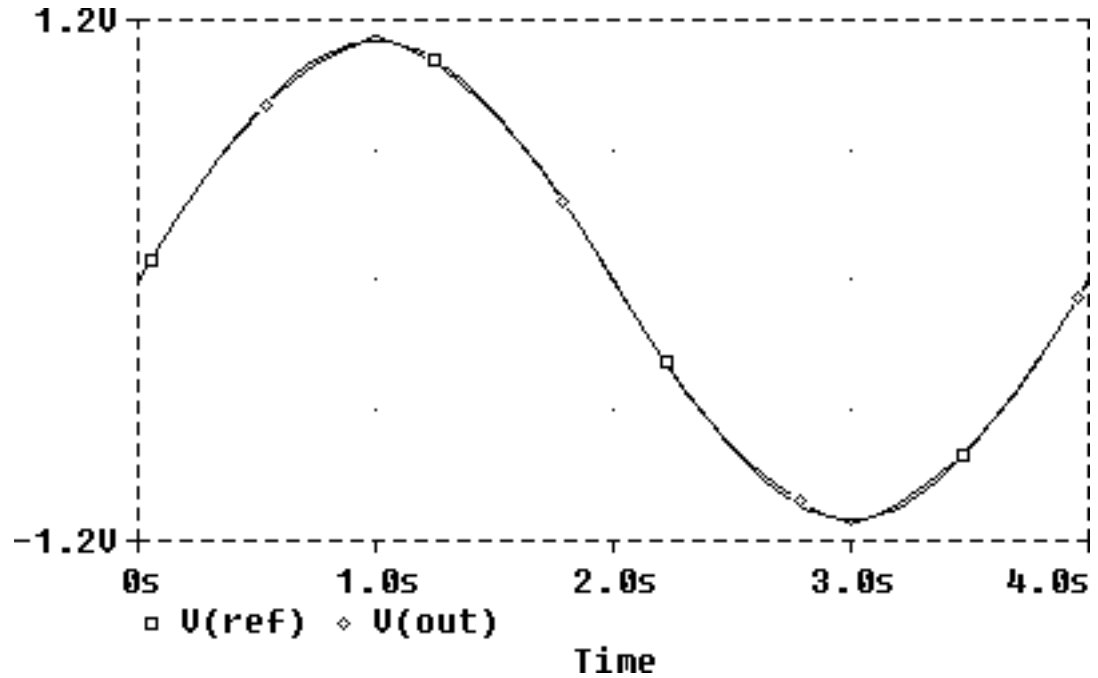

Another comparison of some interest is plotted next; this is a comparison of the triangular waveform against the associated 'sinusoidal' output.

